


Calvin Roberts

Lab Circuits Step Response

EN-01 11/28

Experiment 1

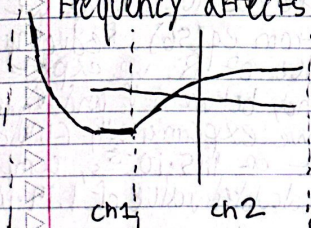
We are doing this experiment to observe how frequency affects voltage on the oscilloscope.



We observe (to the left) on the oscilloscope. The max val is 2V.

At a higher frequency the lines increase in number on the screen to beyond the pixel limit of the oscilloscope. At a lower frequency the curve stretches to almost a flat line across the screen.


$V_R(t)$

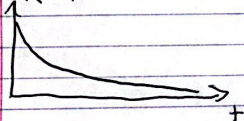

We expect $V_R(t)$ to look like (to the left).

Experiment 2

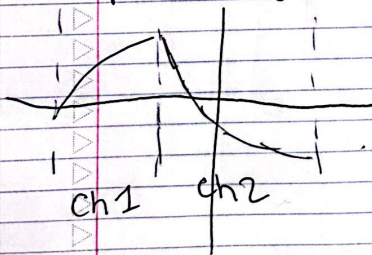We are doing this experiment to further investigate waveforms on an oscilloscope. What we see below



matches our previous prediction. We observe 8 μ s reading on cursor 1 when channel 1 drops from 2V to 1V, and a 4 μ s reading on cursor 2 when channel 2 drops from 2V to 1V. We measured a time constant $1.443 \cdot 8 \cdot 10^{-6} = 1.15 \cdot 10^{-5}$ s, compared to our theoretical time constant $1200 \Omega \cdot 9.9 \cdot 10^{-9} \text{ F} = 1.19 \cdot 10^{-5}$ s. The time constant will decrease as R decreases, and increase as C increases. The circuit will charge/discharge faster as the time constant decreases.

Experiment 3

We are doing this experiment to further investigate circuit step responses. We observe on the oscilloscope what we would expect from eq (56). Reducing the value of R , we expect



the discrepancy between V_o and V_{max} to increase. We experimentally find a time constant of $1.15 \cdot 10^{-5} s$, compared with our R_L calculated value of $1.19 \cdot 10^{-5} s$.

Pre Lab

SN-01 11/28

$$1. \tau = 1200 \cdot 10 \cdot 10^{-9} = \boxed{1.2 \cdot 10^{-5} \text{ s}}$$
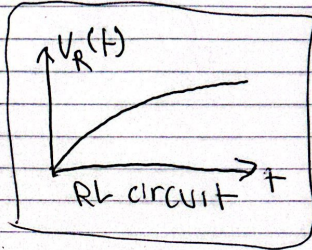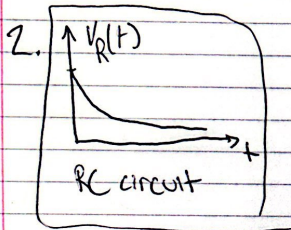
$$\tau = \frac{15 \cdot 10^{-3}}{1200 + 130} = \boxed{1.13 \cdot 10^{-5} \text{ s}}$$



$$3. \frac{V_0}{2} = V_0(1 - e^{-t/\tau})$$

$$\frac{1}{2} = e^{-t/\tau}$$

$$\ln(2) = \frac{t_{1/2}}{\tau}$$

$$\tau = \frac{t_{1/2}}{\ln(2)} = \boxed{1.443 t_{1/2}}$$