CSE100 Lab 2 – Arithmetic Logic Unit

Contents

1	Submission	1
2	Goals	1
3	Prelab	2
4	Lab	3

Copyright © 2024 Ethan Sifferman.

All rights reserved. Distribution Prohibited.

1 Submission

- Due: Tuesday 7/09/2024 end of lab section.
- Submit your Prelab answers to Gradescope.
- Submit your code to the Gradescope autograder. (You have unlimited submission attempts).
- Demonstrate your implementation to a TA.

2 Goals

You will implement an Arithmetic Logic Unit, capable of doing addition, subtraction, square root, and base 2 logarithms.

Once you finish your implementation, you will program it to a Basys 3 FPGA Board.

3 Prelab

1. Find first set

A common hardware operation is called "find first set"; (https://en.wikipedia.org/wiki/Find_first_set). This operation should return the index of the most-significant 1 in a binary number. For example, FFS(0b1)==0, FFS(0b100)==2, FFS(0b100101)==5. Note that this operation also performs |log₂|.

Draw out a circuit diagram of how to implement "find first set" using MUXes, up to a word length of 8 bits. Assume FFS(0b0)==0. You may use an ellipsis (...) to denote repeated cells.

2. Square-root Lookup Table

Large, custom lookup tables are common in hardware design. Some operations are very slow and complicated to compute, so it is be beneficial to precompute them and store the results in a large read-only memory (ROM).

FPGAs have large blocks of memory called Block-RAM (BRAM), which can emulate a ROM. You can initialize the ROM by loading a ".memh" file into an array using \$readmemh from IEEE 1800-2023, Section 21.4; https://ieeexplore.ieee.org/document/10458102.

You are provided a script, "rtl/generate_sqrt_lut.py", which automatically generates a "sqrt.memh" file which has a list of precomputed square-roots. Read the Xilinx documentation for further information initializing BRAM: https://docs.amd.com/r/en-US/ug901-vivado-synthesis/Specifying-RAM-Initial-Contents-in-an-External-Data-File.

Answer the following questions. (Be concise).

- a. What dimensions should your SQRT Lookup Table have? (word length × number of words).
- b. What line of code is needed to initialize your BRAM with the precomputed SQRT values?

4 Lab

You need to complete and submit the following files:

- "rtl/flog2.sv"
- "rtl/sqrt.sv"
- "rtl/alu.sv"
- "synth/basys3/Basys3_Master.xdc"
- "synth/basys3/basys3.sv"
- 1. Create a flog2 module inside the file "rtl/flog2.sv", and implement your design you drew in the Prelab. Assume FFS(0b0)==0.
- 2. Create a sqrt module inside the file "rtl/sqrt.sv", and implement the design using a ROM, as specified in the Prelab.
- 3. Finish the alu module in "rtl/alu.sv" according to this operation encoding:

Encoding	Operation
operation==4'b0001	ADD
operation==4'b0010	SUB
operation==4'b0100	FLOG2
operation==4'b1000	SQRT
else	y = 0

The alu module should instantiate flog2 and sqrt and create an adder and subtractor using the + and - operators. Then, a MUX should be used to select between the different operators.

- 4. Complete the Basys3 configuration: according to these specifications:
- The basys3 module inside the file "synth/basys3/basys3.sv" should instantiate and drive an alu.
- The Basys3 constraints file "synth/basys3/Basys3_Master.xdc" was downloaded from Digilent's GitHub: https://github.com/Digilent/Basys3/blob/master/Resources/XDC/Basys3_Master.xdc. Complete it to match your basys3 module.
- The bottom 8 switches should control alu.a_i.
- The top 8 switches should control alu.b i.
- The 4 directional buttons should control alu.operation_i.
- The bottom 8 LEDs should be controlled by alu.y_o.

Refer to Lab 1 and the Basys3 Reference Manual if you have questions: https://reference.digilentinc.com/reference/programmable-logic/basys-3/reference-manual.

- 6. Simulate your design using commands specified in the "README.md". Submit to the autograder until you get 100%.
- 7. Synthesize your design and program it to the Basys3 using commands specified in the "README.md". Get checked off by a TA.