

ECE 101L

LAB 1: Fundamental Circuit Theory Laws

Jan 23, 2024

Caden Roberts: 2082015

Section A

1 Introduction

1.1 Purpose of Experiment

We are doing this experiment to investigate and verify the fundamental laws (and derived quantities) of KVL and KCL. In the first circuit, we will experimentally apply KVL and KCL to a DC circuit to gain theoretical confidence and experimental skill using the lab power supply and digital voltmeter (DVM). The lamp circuit will introduce nonlinear resistances, and we will test current and voltage changes through a circuit with one set lamp.

1.2 Background Theory

Kirchoff's two fundamental Laws, voltage and current, KVL and KCL, form the basis of all circuit theory. Knowing voltages and currents, their ratio gives us the useful property of resistance in Ohms [R or Ω], while their product gives us power flow in watts [W].

The KVL law is:
$$\sum_{k=1}^n V_k = 0$$

The KCL law is:
$$\sum_{k=1}^n I_k = 0$$


1.3 Expected Results

We consider the following circuit:

Nodal Analysis at V_1 :
$$\frac{V_1 - V_{\text{source}}}{R_1} + \frac{V_1}{R_3} + \frac{V_1 - V_2}{R_2} = 0$$

Nodal Analysis at V_2 :
$$\frac{V_2 - V_1}{R_2} + \frac{V_2}{R_{\text{load}}} = 0$$

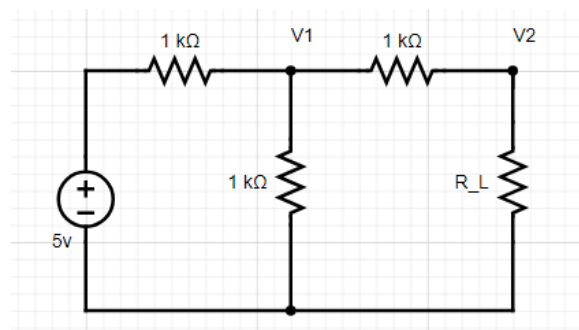Theoretical Values, with R_1 , R_2 , and $R_3 = 1$ are as follows:




R_{load}	V_1	V_2	I_1	I_2	I_3	P_1	P_2	P_3	P_L
k Ω	V	V	mA	mA	mA	mW	mW	mW	mW
0	1.667	0	3.333	1.667	1.667	11.108	2.778	2.778	0
1	2	1	3	1	2	9	1	4	1
10	2.391	2.174	2.609	0.2174	2.391	6.807	0.047	5.717	0.473
100	2.488	2.463	2.51	0.0246	2.488	6.300	0.000605	6.190	0.061

2 Results and Analysis

We build the following circuit for $R_{load} = 0$:

We replace the R_{load} wire with resistors for 1, 10 and 100 k Ω and the circuit remains the same, with actual values of $R_1 = 0.9896$, $R_2 = 0.9859$, and $R_3 = 0.9866$.

Experimental Values are as follows:

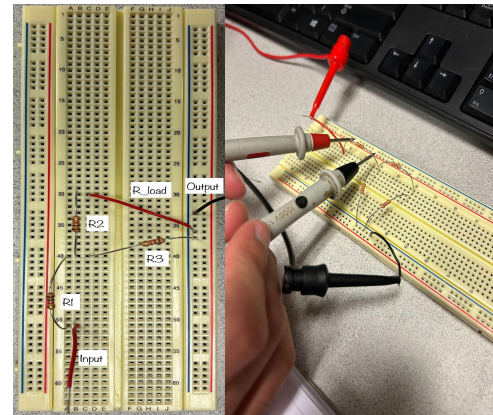

R_{load}	V_1	V_2	I_1	I_2	I_3	P_1	P_2	P_3	P_L
k Ω	V	V	mA	mA	mA	mW	mW	mW	mW
0.0001	1.667	0.0001	3.3357	1.680	1.6791	11.127	2.8224	2.8194	0.0003
0.987	2.0682	1.0341	2.9318	1.0341	1.8977	8.595	1.069	3.6012	1.069
9.653	2.3879	2.1637	2.6121	0.224	2.3831	6.823	0.0502	5.8636	0.5017
95.687	2.4871	2.4613	2.513	0.0257	2.4786	6.3152	0.000662	6.143	0.065536

3 Error Analysis

With % error calculated as follows, $\% \text{ Error} = 100 \times \frac{\text{Calculated} - \text{Measured}}{\text{Calculated}}$, we find:

$R_{\text{load}} \text{ k}\Omega$	Value	Theoretical	Measured	% Error
0	$V_1 \text{ V}$	1.667	1.667	0
0	$V_2 \text{ V}$	0	0	100
0	$I_1 \text{ mA}$	3.333	3.33357	0.0072
0	$I_2 \text{ mA}$	1.667	1.680	0.78
0	$I_3 \text{ mA}$	1.667	1.6791	0.73
0	$P_1 \text{ mW}$	11.108	11.127	0.17
0	$P_2 \text{ mW}$	2.778	2.8224	1.598
0	$P_3 \text{ mW}$	2.778	2.8194	1.49
0	$P_L \text{ mW}$	0	0.0003	100

$R_{\text{load}} \text{ k}\Omega$	Value	Theoretical	Measured	% Error
1	$V_1 \text{ V}$	2	2.0682	3.41
1	$V_2 \text{ V}$	1	1.0341	3.41
1	$I_1 \text{ mA}$	3	2.9318	2.27
1	$I_2 \text{ mA}$	1	1.0341	3.41
1	$I_3 \text{ mA}$	2	1.8977	5.12
1	$P_1 \text{ mW}$	9	8.595	4.5
1	$P_2 \text{ mW}$	1	1.069	6.9
1	$P_3 \text{ mW}$	4	3.6012	9.97
1	$P_L \text{ mW}$	1	1.069	6.9



$R_{\text{load}} \text{ k}\Omega$	Value	Theoretical	Measured	% Error
10	$V_1 \text{ V}$	2.391	2.3879	0.13
10	$V_2 \text{ V}$	2.174	2.1637	0.474
10	$I_1 \text{ mA}$	2.609	2.6121	0.119
10	$I_2 \text{ mA}$	0.2174	0.224	3.036
10	$I_3 \text{ mA}$	2.391	2.3831	0.33
10	$P_1 \text{ mW}$	6.807	6.823	0.235
10	$P_2 \text{ mW}$	0.047	0.0502	6.809
10	$P_3 \text{ mW}$	5.717	5.8636	2.564
10	$P_L \text{ mW}$	0.473	0.5017	6.068

$R_{\text{load}} \text{ k}\Omega$	Value	Theoretical	Measured	% Error
100	$V_1 \text{ V}$	2.488	2.4871	0.0036
100	$V_2 \text{ V}$	2.463	2.4613	0.069
100	$I_1 \text{ mA}$	2.51	2.513	0.12
100	$I_2 \text{ mA}$	0.0246	0.0257	4.472
100	$I_3 \text{ mA}$	2.488	2.4786	0.378
100	$P_1 \text{ mW}$	6.300	6.3152	0.241
100	$P_2 \text{ mW}$	0.000605	0.000662	9.421
100	$P_3 \text{ mW}$	6.190	6.143	0.759
100	$P_L \text{ mW}$	0.061	0.000662	7.436

Part II

We observe the following lamp circuit:

Experimental values are as shown:

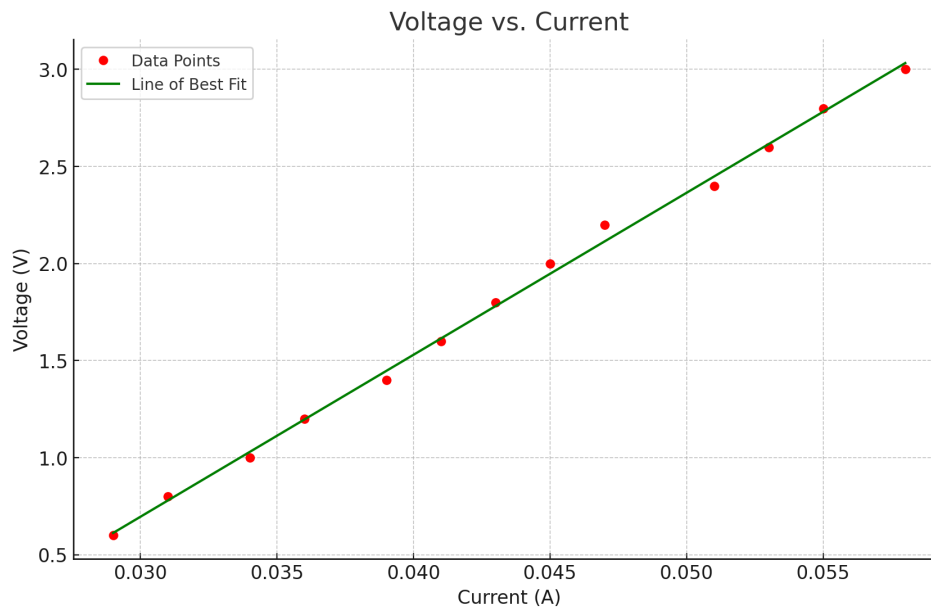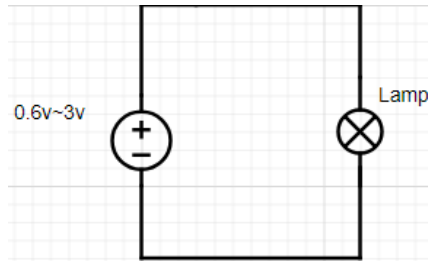

Voltage	Current
0.6v	0.029A
0.8v	0.031A
1v	0.034A
1.2v	0.036A
1.4v	0.039A
1.6v	0.041A
1.8v	0.043A
2v	0.045A
2.2v	0.047A
2.4v	0.051A
2.6v	0.053A
2.8v	0.055A
3v	0.058A

Conclusion

Through this lab we learned nodal analysis alongside the KVL and KCL laws. We used breadboards, resistors, and wires to run our experimental values after calculating theoretical values of voltage, current, and power dissipated for the given circuit, where we observed a relatively small % error. We then observed current as voltage changes through a simple lamp circuit, finding a linear and positively-correlated relationship.